

Formule iz Osnova Elektrotehnike

koje se mogu koristiti na međuispitima i završnom ispitu – III dio (2009/2010)

Teoremi:

$$\dot{U}_{12} = \frac{\sum_{i=1}^n (\dot{E}_i Y_i + \dot{I}_i)}{\sum_{i=1}^n Y_i}$$

$$\dot{E}_T = \underline{Z}_T \dot{I}_N$$

$$\underline{Z}_T = \underline{Z}_N$$

Trofazni sustav:

spoj u zvijezdu:

$$U_l = \sqrt{3} U_f$$

$$I_l = I_f$$

spoj u trokut:

$$I_l = \sqrt{3} I_f$$

$$U_l = U_f$$

$$P_{uk} = 3P_f = 3U_f I_f \cos(\varphi) = \sqrt{3} U_l I_l \cos(\varphi)$$

$$\dot{U}_{0'0} = \frac{\dot{U}_{R0} \underline{Y}_R + \dot{U}_{S0} \underline{Y}_S + \dot{U}_{T0} \underline{Y}_T}{\underline{Y}_R + \underline{Y}_S + \underline{Y}_T}$$

Efektivne i srednje vrijednosti:

$$Y_{ef} = \sqrt{\frac{1}{T} \int_0^T y(t)^2 dt}$$

$$Y_{sr} = \frac{1}{T} \int_0^T y(t) dt$$

$$\xi = \frac{Y_{ef}}{Y_{sr}} \quad \sigma = \frac{Y_m}{Y_{ef}}$$

$$Y_{ef} = \sqrt{Y_0^2 + Y_{1ef}^2 + Y_{2ef}^2 + \dots}$$

$$Y_{sr} = Y_{sr0} \frac{T_i}{T}$$

$$Y_{ef} = Y_{ef0} \sqrt{\frac{T_i}{T}}$$

Nesinusoidne pobude u el. krugu:

$$P = P_0 + P_1 + P_2 + \dots + P_n$$

$$I_{ef} = \sqrt{I_0^2 + I_{1ef}^2 + I_{2ef}^2 + \dots + I_{nef}^2}$$

$$U_{ef} = \sqrt{U_0^2 + U_{1ef}^2 + U_{2ef}^2 + \dots + U_{nef}^2}$$

Prijelazne pojave – kondenzator:

$$\tau = RC$$

$$u_C(t) = U(1 - e^{-\frac{t}{\tau}})$$

$$i(t) = \frac{U}{R} e^{-\frac{t}{\tau}}$$

Prijelazne pojave – induktivitet:

$$\tau = \frac{L}{R}$$

$$u_L(t) = U e^{-\frac{t}{\tau}}$$

$$i(t) = \frac{U}{R} (1 - e^{-\frac{t}{\tau}})$$